

EXPERIMENT 2

CLIPPING CIRCUITS


EQUIPMENT REQUIRED:

- Diode-IN4007, capacitors, resistor, power supply, oscilloscope, function generator, multimeter, etc.
- Choose $R_f=10\Omega$, $R_r=1M\Omega$ $R=\sqrt{R_f R_r}=3.3K\Omega$


EXPERIMENTAL PROCEDURE:

- Connections are made as shown in the circuit diagram.
- A sine wave input V_i whose amplitude is greater than the clipping level is applied.
- Output waveform V_o is observed on the oscilloscope.
- Clipped voltage is measured and verified with the designed values.

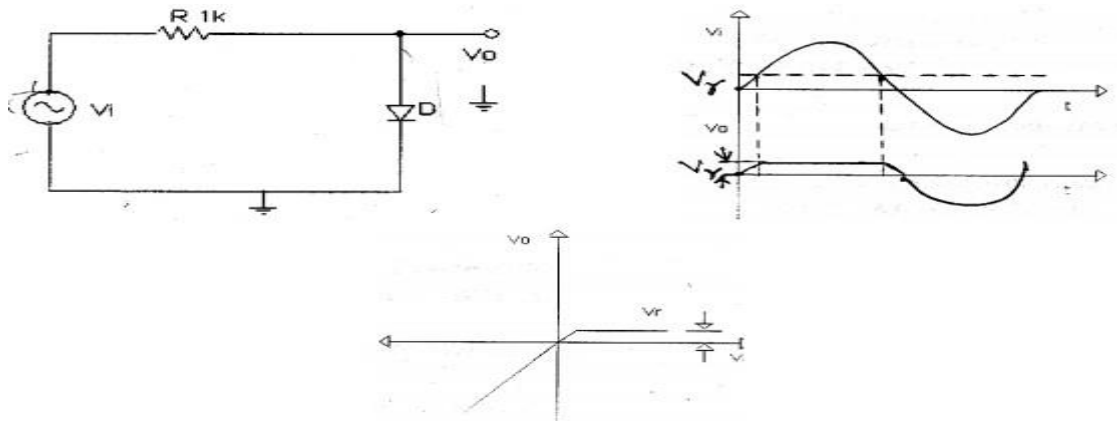
1. To Remove Positive Voltage Peak Above $+V_y$ Level



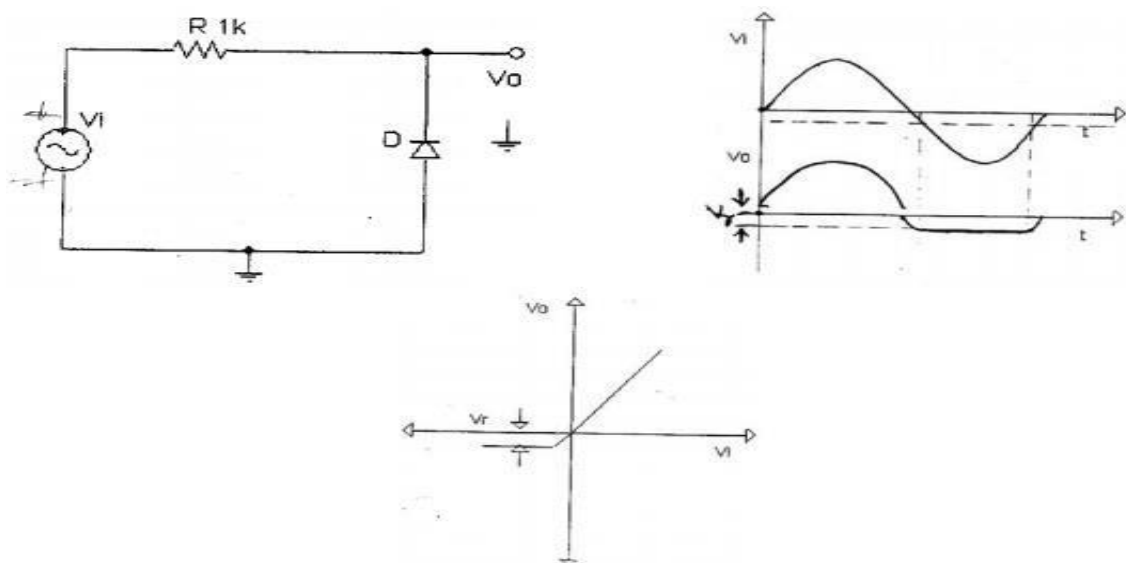
2. To Remove Negative Voltage Peak Below $-V_y$ Level:



3. Adding Extra DC Voltage Source (+5V)

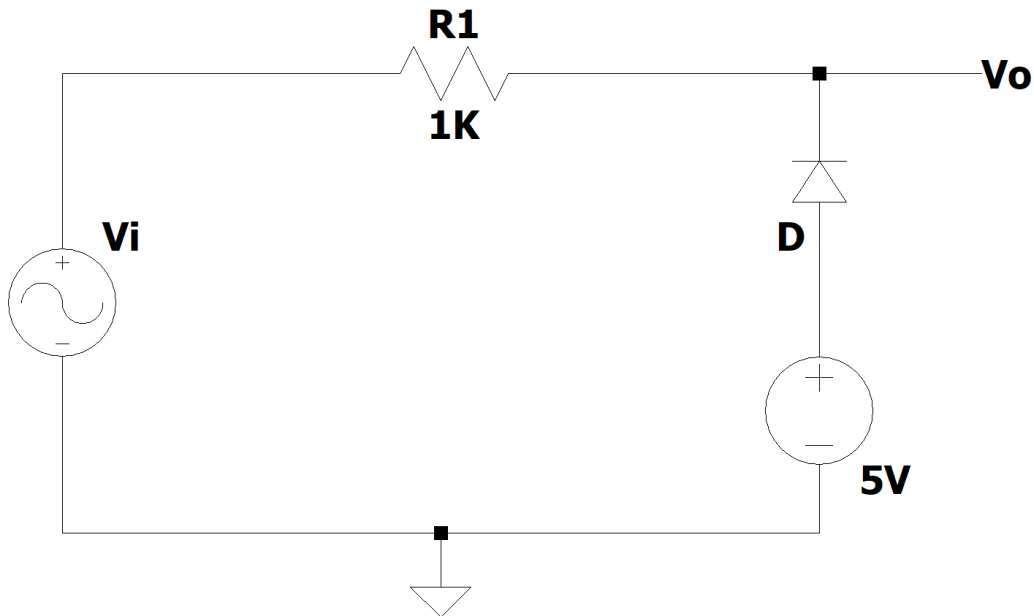

4. Adding Extra DC Voltage Source (-5V)

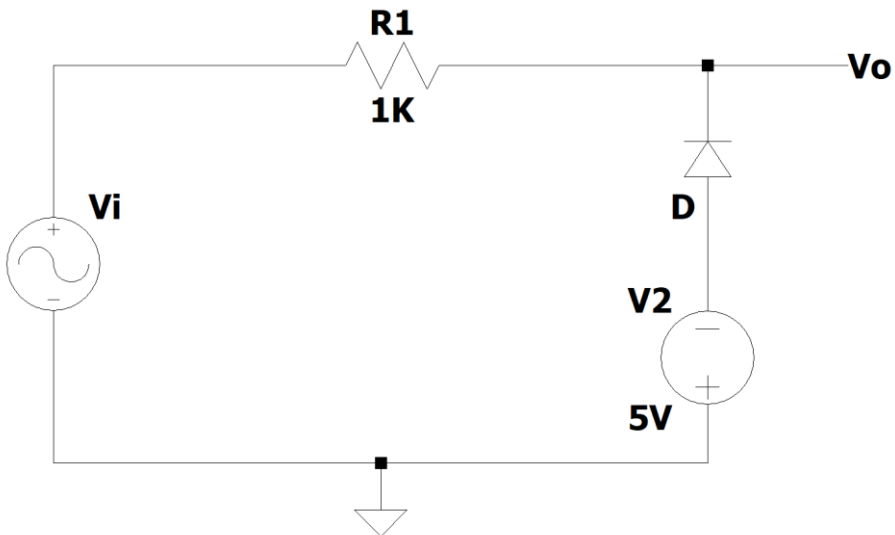

QUESTIONS:

1. What could happen if the diode's type would be changed from silicon to germanium?
2. Try to explain the logic behind the result of circuits 3 and 4.
3. Why a diode act like an open circuit? In which circumstances this occur?